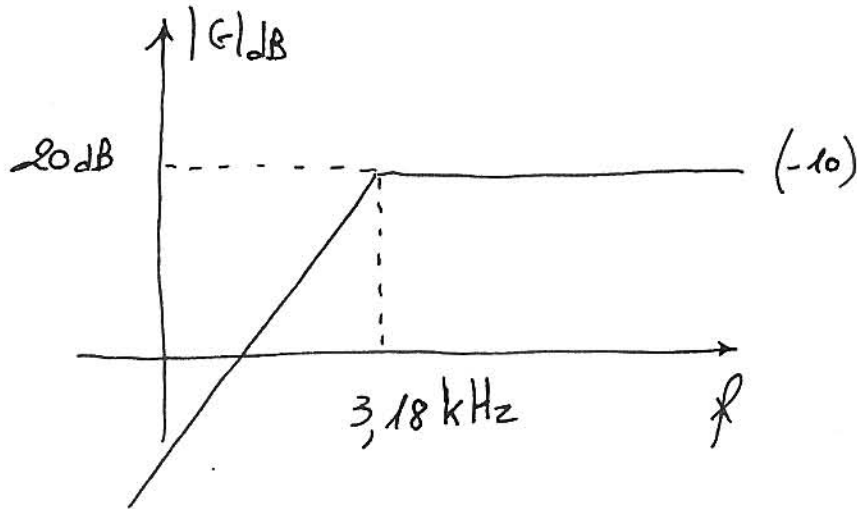


est

$$a) \quad G = - \frac{Z_2}{Z_1} = - \frac{SC_1 R_2}{1 + SC_1 R_1}$$



PASSA  
ALTO


$$b) \quad Z_{IN} = \frac{1 + SC_1 R_1}{SC_1}$$

$$c) \quad V_{OUT, \text{offset}} = 2 \text{ mV}$$


$$V_{OUT, I_{BIAS}} = 5 \text{ mV} \quad \left( \begin{array}{l} \text{SUPPONENDO} \\ \text{correnti entranti} \end{array} \right)$$

$$d) \quad G_{loop} = - \frac{10^5}{1 + S\tau_{op}} \frac{1 + SC_1 R_1}{1 + SC_1 (R_1 + R_2)}$$
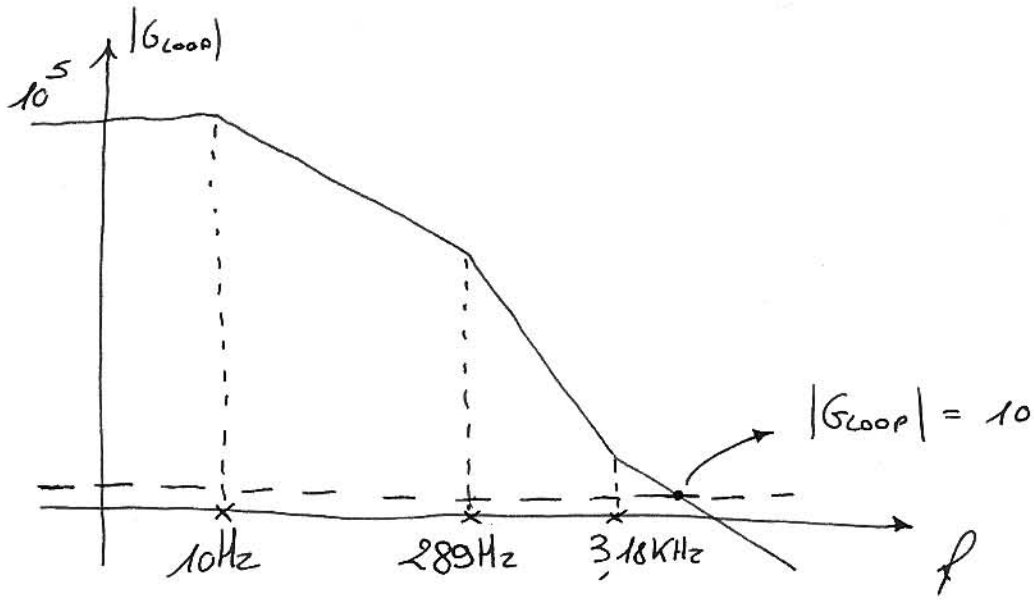
$$\frac{1}{2\pi\tau_{op}} = 10 \text{ Hz}$$



e)  $f_{MAX} \approx 9,1 \text{ kHz}$

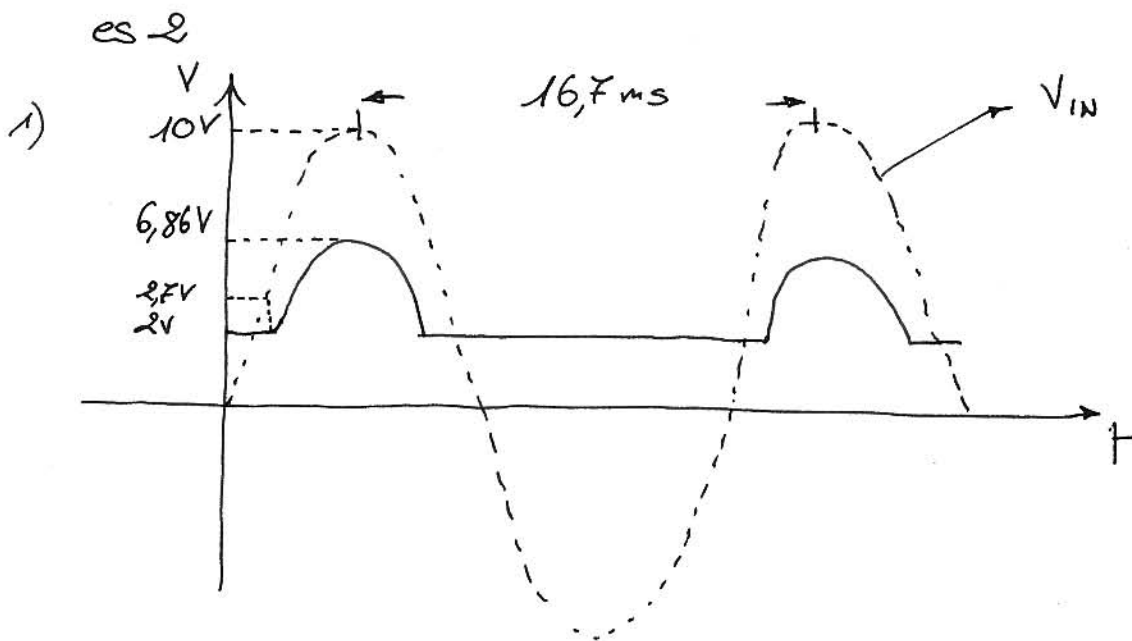


$D_1 \text{ OFF} \rightarrow V_{OUT} = 2V$

$D_1 \text{ ON} \rightarrow V_{OUT} = 2V + \frac{2}{3} (V_{IN} - 2,7) = \frac{2}{3} V_{IN} + 0,2V$

$D_2 \text{ sempre OFF}$

es

2)

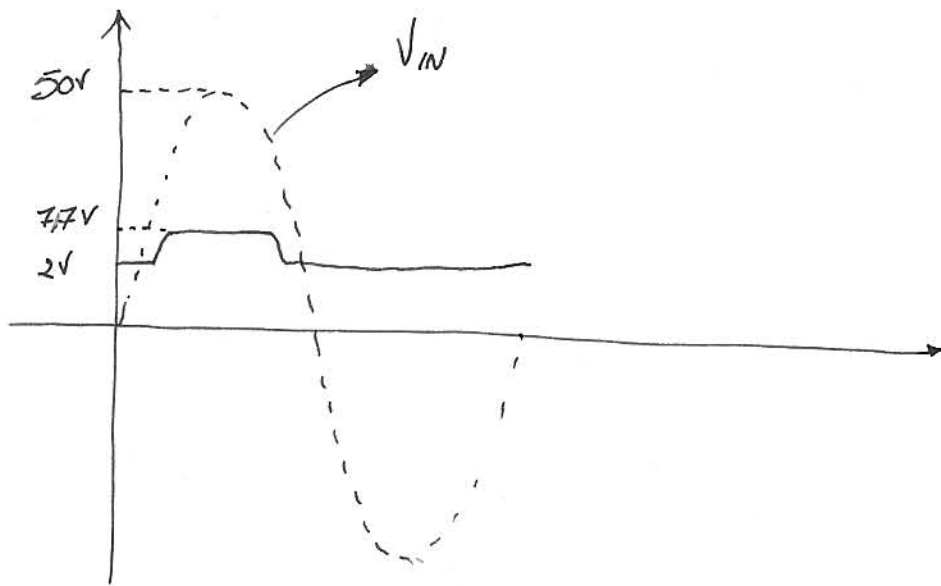

Per  $V_{IN} > 11,25V$  De ON e  $V_{OUT} = 7,7V$

es 3

1)  $V_G = -1V$   
 $V_S = -4V$   $I_D = 1mA$   
 $V_D = 1V = V_{OUT}$  MOS saturazione

2)  $G = \frac{v_{out}}{v_{in}} = -2$

3)  $G = \frac{v_{out}}{v_{in}} = -1$

4) → IL MOS ra in zona ohmica

$$V_{IN, MAX} = +1V$$

es 4

A	B	C
1	0	1
1	1	0
0	1	0
0	0	0

