

Sensors, Signals and Noise

COURSE OUTLINE

- Introduction
- Signals and Noise
- **Filtering: LPF1 Constant-Parameter Low Pass Filters**
- Sensors and associated electronics



Constant-Parameter Low-Pass Filters

- Low-Pass Filters as Basic Elements for Signal and Noise Filtering
- RC Integrator
- Mobile-Mean Low-Pass Filter
- Bandwidth and Correlation Time of Low-Pass Filters



Low-Pass Filters as Basic Elements for Signal and Noise Filtering



Filtering signals and noise

SIGNALS AND NOISE

- Signals carry information, but are accompanied by noise
- The noise often is non-negligible and can degrade or even obscure the information
- Filtering is intended to improve the recovering of the information
- Filtering must **exploit** at best the **differences** between signal and noise, taking well into account **what kind of information** is to be recovered. For instance: in case of a pulse-signal, is it just the amplitude or is it the complete waveform?

LOW-PASS FILTERS

- We deal first with «low-pass filters» (LPF), so called because of their action in the frequency domain. The filtering weight is concentrated in a **relatively narrow frequency band** from zero to a limit frequency; above the band-limit it falls to negligible value.
- Correspondingly, in the time domain the weighting function has **relatively wide time-width** (as well as its autocorrelation).
- The action of the filter as seen in time-domain is to produce approximately a **time-average** (i.e. a weighted average) of the input over a finite time interval, delimited by the width of the weighting function



Low-pass filters LPF

To understand and to be able to deal with LPF is very important because:

- a) LPF are a **basic element** of filtering and a **foundation** for gaining a better insight on all other kinds of filters and better exploit them.

For instance, a high-pass filter (HPF) can be obtained by subtracting from a given input the output of an LPF that receives the same input. In various real HPF, the physical structure of the HPF actually implements this scheme.

- b) LPF are **employed in real cases** of filtering for information recovery

For instance, in many cases a wide-band noise accompanies signals that have significant frequency components in a relatively narrow frequency band around $f=0$.


These are not only the cases of DC and slowly varying signals, but also cases where the just the **amplitude** of a **pulse signal** (having fairly long pulse-duration and known pulse shape) must be measured (and not the complete waveform)



RC-integrator




RC integrator (constant-parameter LPF)

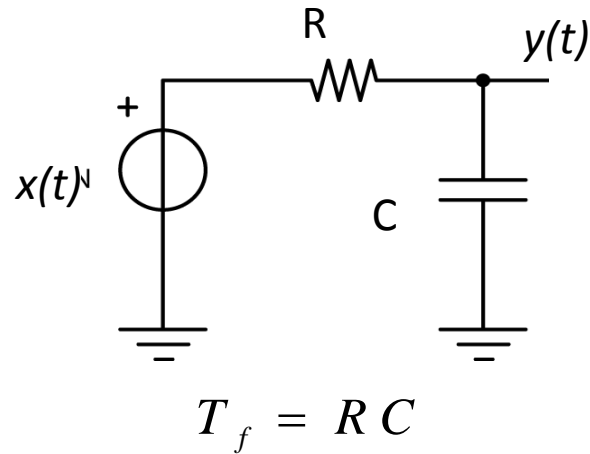

δ -response

$$h(t) = \frac{1}{T_f} 1(t) e^{-t/T_f}$$

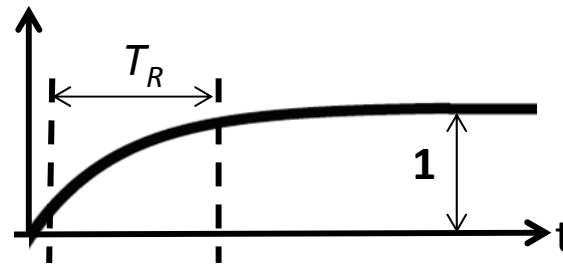

Step-response
with


risetime 10-90%

$$T_R = 2.2 T_f \approx 1/3 f_p$$


Transfer function

$$H(f) = \frac{1}{1 + j2\pi f T_f}$$


$$|H(f)|^2 = \frac{1}{1 + (2\pi f T_f)^2}$$

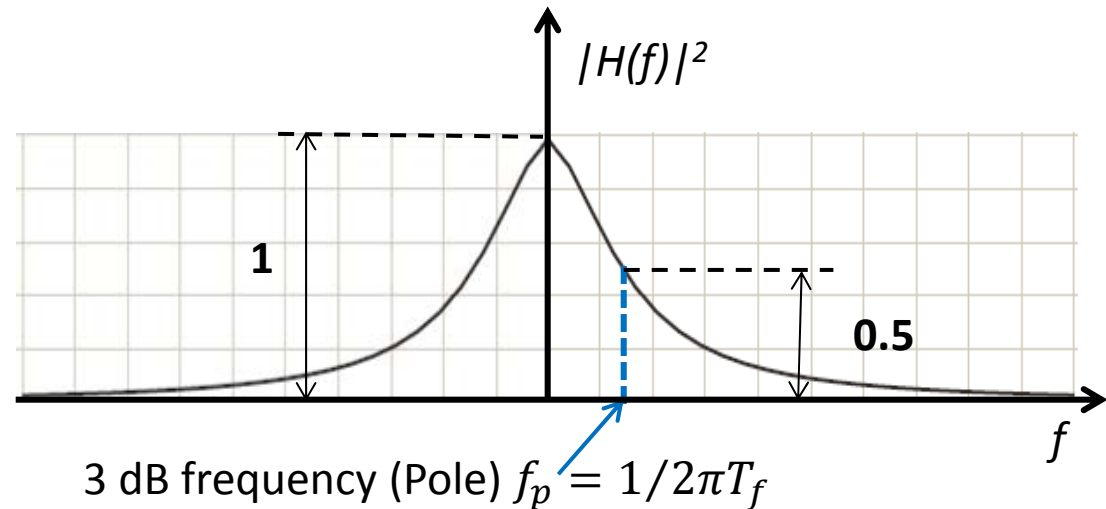

RC integrator: viewpoints on $|H(f)|^2$

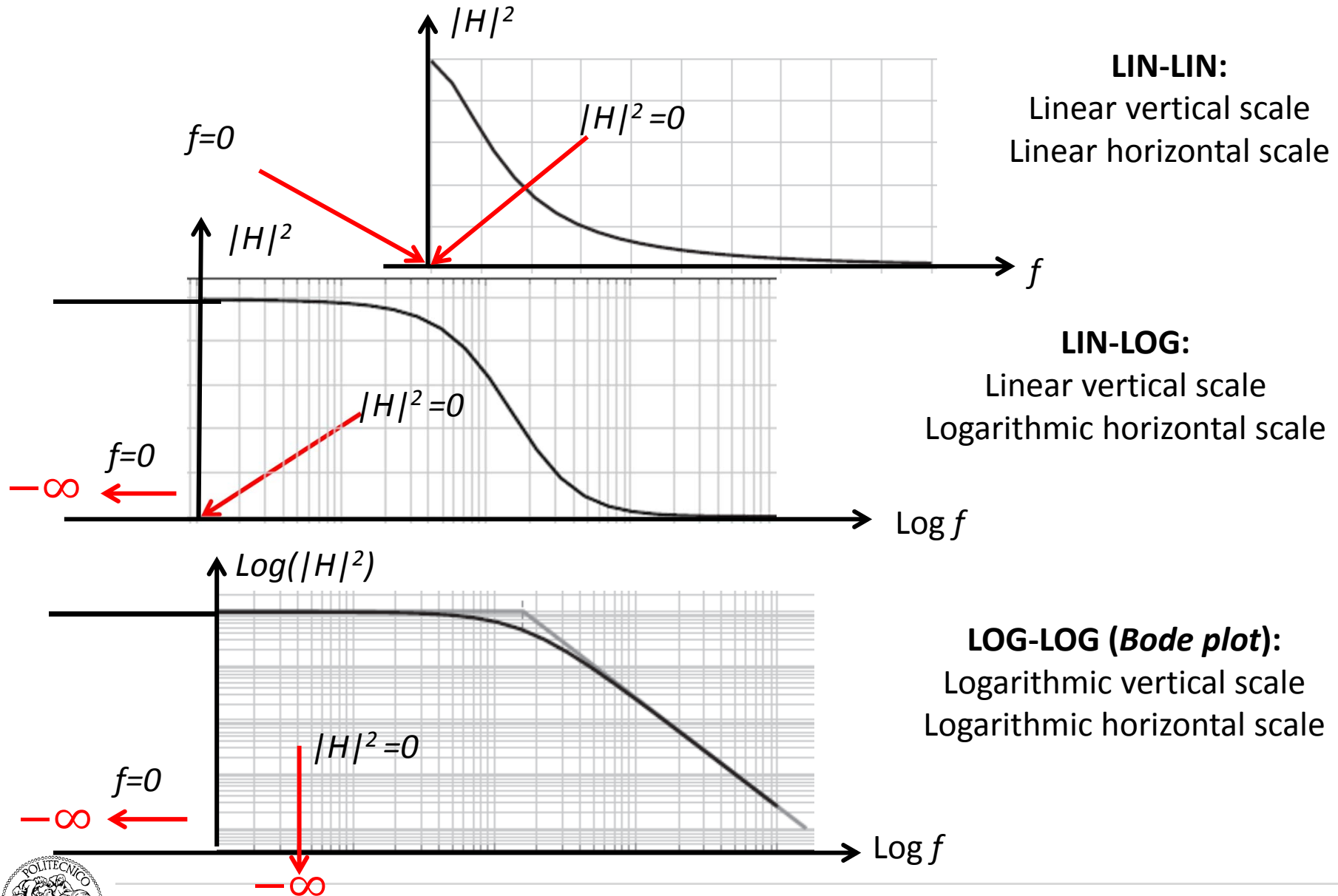


RC integrator (constant-parameter LPF)

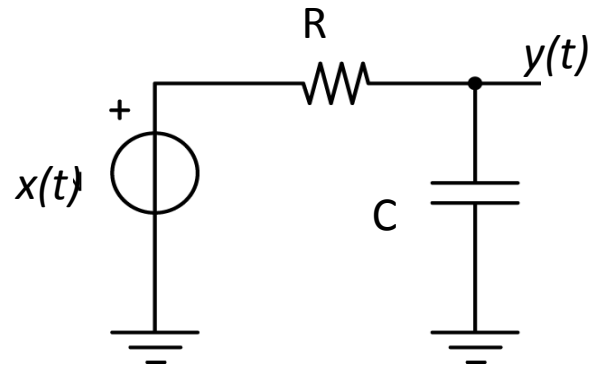

Weighting function
in time

$$w_m(\alpha) = h(t_m - \alpha)$$

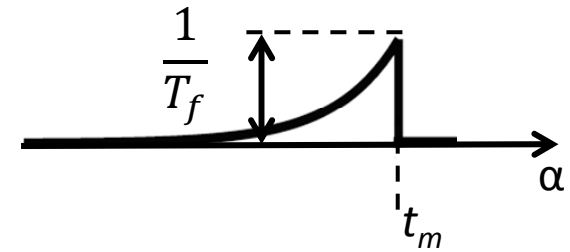


Output: can be seen as an **average over a time interval** $\approx 2T_f$ preceding t_m

Weighting function
in frequency

$$|W_m(f)|^2 = |H(f)|^2$$

$$|W_m(f)|^2 = \frac{1}{1 + (2\pi f T_f)^2}$$

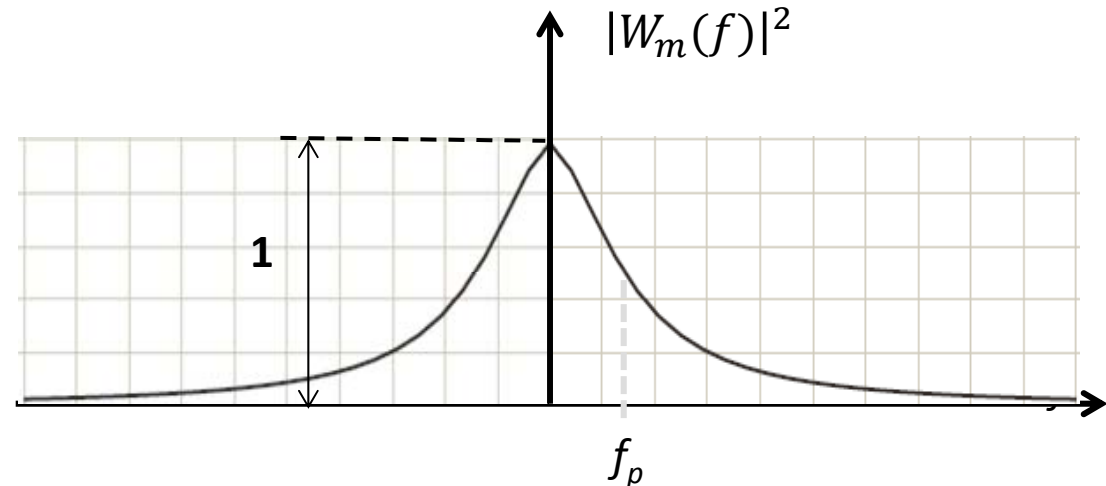


Output: can be seen as a **selection of the lower frequency components** up to $\approx f_p$



RC integrator: filtering wide-band noise

Time-domain analysis

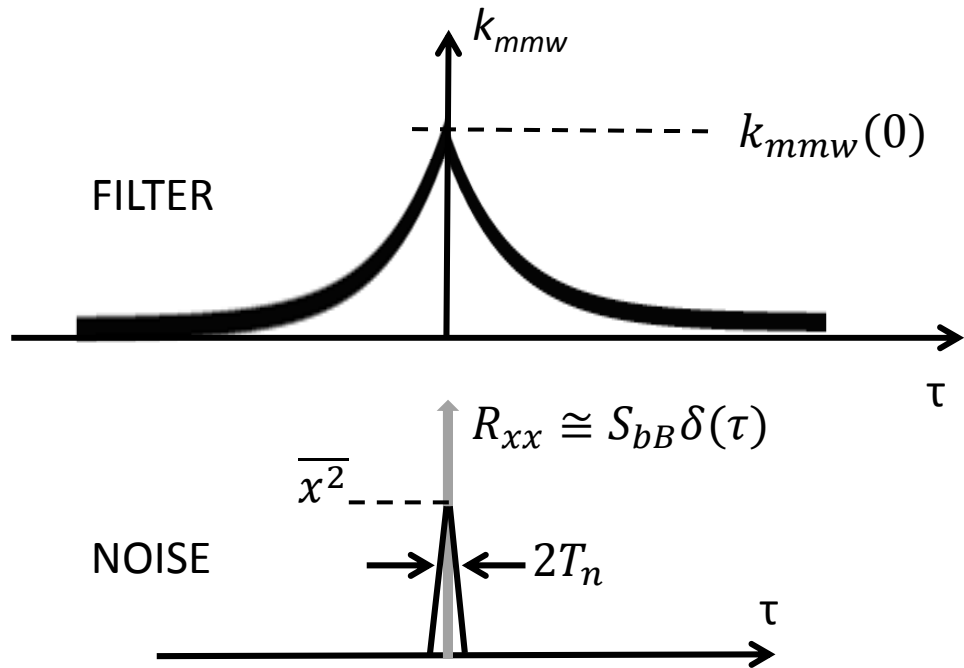

$$k_{mmw}(\tau) = \frac{1}{2T_f} e^{-\left|\frac{\tau}{T_f}\right|}$$

$$\overline{y^2} = \int_{-\infty}^{\infty} R_{xx}(\tau) \cdot k_{mmw}(\tau) d\tau$$

The noise is considered wide-band if it has autocorrelation much narrower than the filter weight autocorrelation, that is, if $T_n \ll T_f$


We can then approximate $R_{xx} \cong S_{bB} \delta(\tau)$ and obtain

$$\overline{y^2} = S_{bB} \cdot k_{mmw}(0) = \frac{S_{bB}}{2T_f}$$



RC integrator: filtering wide-band noise

Frequency-domain analysis

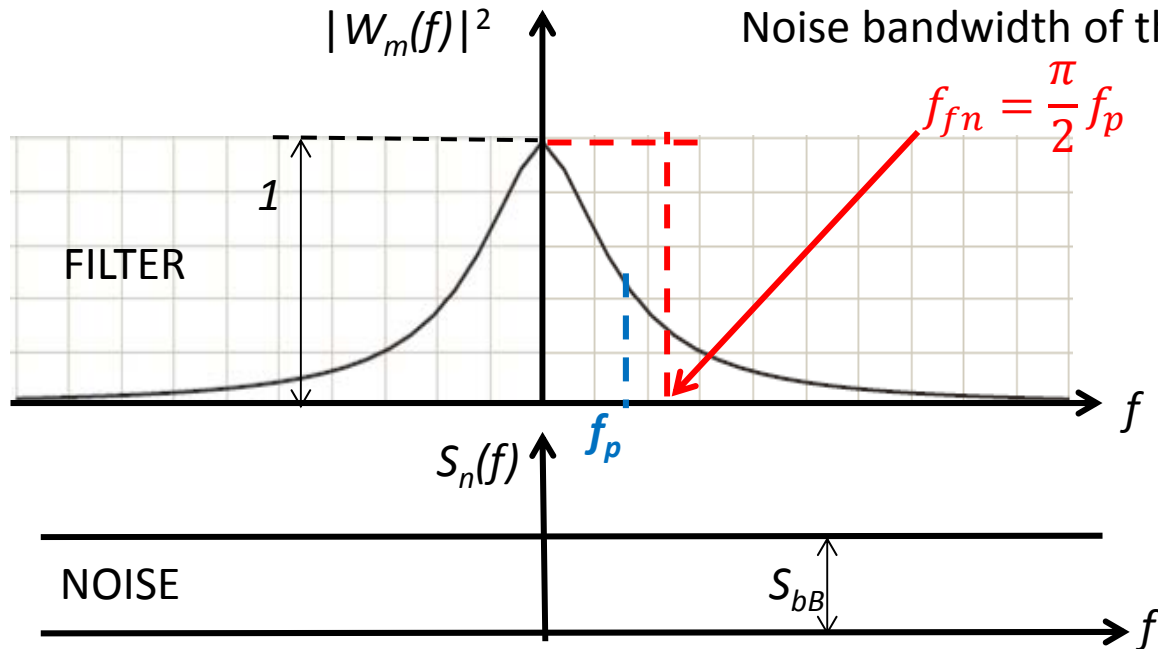

$$|W_m(f)|^2 = |H(f)|^2 = \frac{1}{1 + (2\pi f T_f)^2}$$

$$\overline{y^2} = \int_{-\infty}^{\infty} S_x(f) \cdot |W_m(f)|^2 df$$

The noise is considered wide-band if it has spectrum much wider than the filter weighting spectrum, that is, if its bandlimit $f_n \gg f_p$

We can then approximate $S_x(f) \cong S_{bB}$ and obtain

$$\overline{y^2} = S_{bB} \cdot \int_{-\infty}^{\infty} |W_m(f)|^2 df = S_{bB} \cdot k_{mmw}(0) = \frac{S_{bB}}{2T_f} = S_{bB} \cdot 2f_{fn}$$



RC integrator: noise band-width

Noise bandwidth f_{fn} of the filter:

defined with reference to a white noise input S_b as the bandwidth value to be employed for computing **simply by a multiplication** the output mean square noise

$$\overline{y^2} = S_{bB} \cdot 2f_{fn}$$

Since it is

$$\overline{y^2} = S_{bB} \cdot \int_{-\infty}^{\infty} |W_m(f)|^2 df = S_{bB} \cdot k_{mmw}(0)$$

for any LPF the correct bandwidth limit f_{fn} is

$$f_{fn} = \frac{k_{mmw}(0)}{2}$$

and in particular for the RC integrator

$$f_{fn} = \frac{1}{4T_f} = \frac{\pi}{2} f_p$$



RC integrator: autocorrelation width

Autocorrelation width T_{fn} of the filter:

defined with reference to a white noise input S_b as the value to be employed for computing **simply by a division** the output mean square noise

$$\overline{y^2} = S_{bB} \cdot \frac{1}{2T_{fn}}$$

Since it is

$$\overline{y^2} = S_{bB} \cdot \int_{-\infty}^{\infty} |W_m(f)|^2 df = S_{bB} \cdot k_{mmw}(0)$$

for any LPF we have

$$\frac{1}{2T_{fn}} = k_{mmw}(0)$$

and in particular for the RC integrator


$$T_{fn} = T_f = \frac{1}{4f_{fn}}$$

Note that

$$2f_{fn} \cdot 2T_{fn} = 1$$



RC integrator active filter

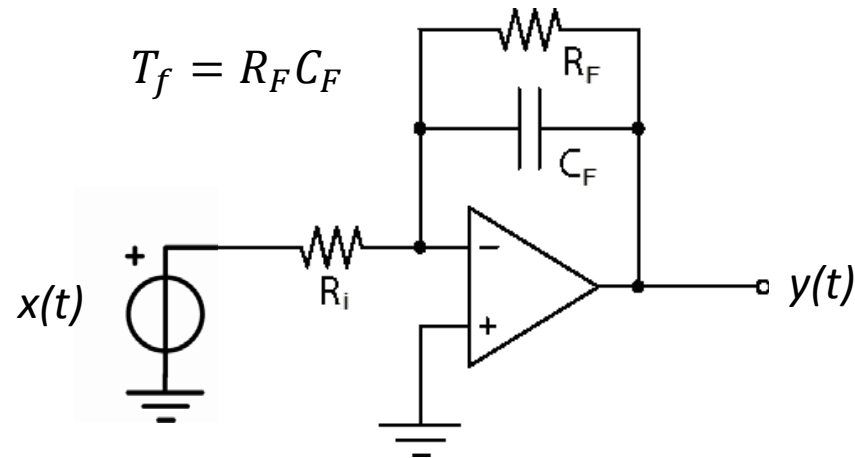

TIME DOMAIN

$$-h(t) = \frac{R_F}{R_i} \frac{1}{T_f} 1(t) e^{-t/T_f}$$



$$w_m(\alpha) = h(t_m - \alpha)$$

FREQUENCY DOMAIN

$$|H(f)|^2 = \left(\frac{R_F}{R_i}\right)^2 \frac{1}{1 + (2\pi f T_f)^2}$$

$$|W_m(f)|^2 = |H(f)|^2$$


$$\text{dc gain } |W_m(0)| = \frac{R_F}{R_i}$$

In comparison with the passive RC:

- still a constant-parameter filter
- same shape of the weighting
- dc gain = $\frac{R_F}{R_i}$ instead of 1



Rather RC-averager than RC-integrator

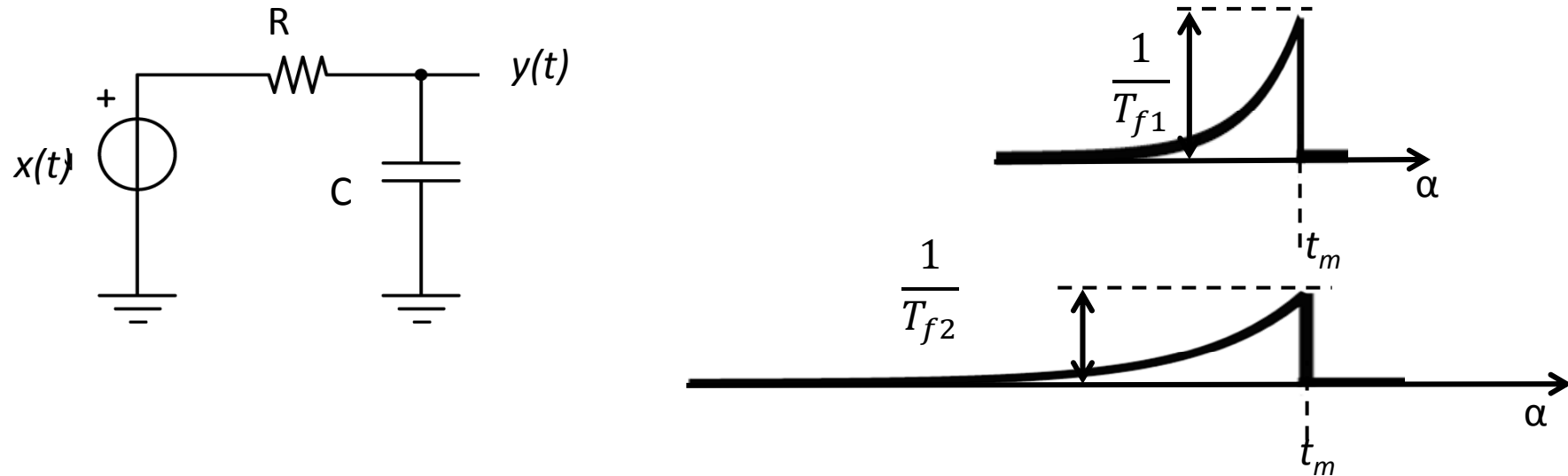

- When T_f is changed the dc gain does NOT change, the area of $w_m(\alpha)$ is always unity.
- When T_f is made longer the weight is extended in time but becomes lower (see figure)
- With any T_f setting, the output is an average of the input (weighted) over a time interval $\approx 2T_f$ preceding t_m

The conclusion is valid also for the active filter configuration :


When T_f of the filter is changed keeping constant the dc gain of the amplifier (i.e. with constant ratio R_F/R_i) the output is always an average of the input (weighted) over a time interval $\approx 2T_f$ preceding t_m



Mobile-Mean Low-Pass Filter




Mobile-Mean Filter

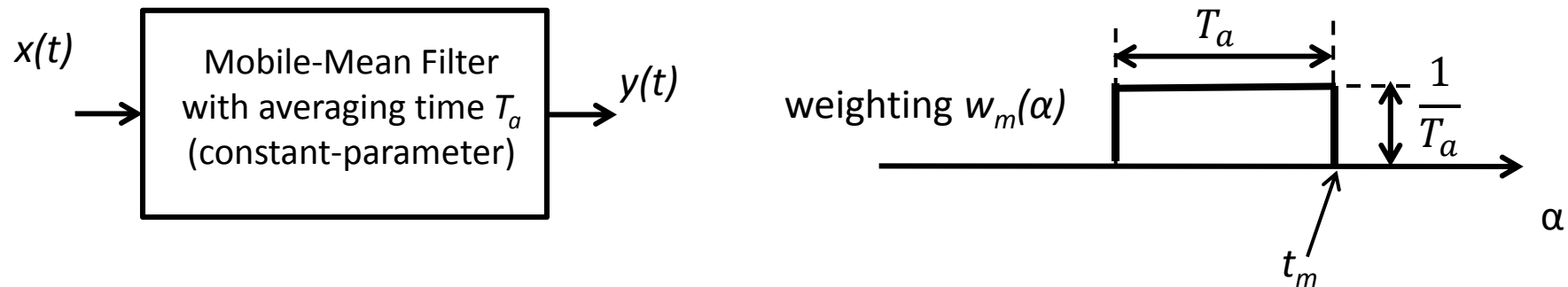


- A mobile-mean filter (MMF) produces at any time t_m an output $y(t_m)$ which is not just the integral of the input $x(t)$ over a time interval T_a that precedes t_m , but rather the **mean** value of the input $x(t)$ **over the time interval T_a** , that is, the integral over T_a **divided by T_a**
- In order to obtain this, if we vary the averaging time T_a we must vary inversely the **weight $1/T_a$** (this ensures constant area of $w_m(\alpha)$ i.e. constant DC gain).
- Note the similarity of the MMF to the RC integrator, which also produces a sort of mobile mean of the input over a few RC (recall that a passive RC filter has inherently constant DC gain, i.e. inherently is an averager)
- The MMF is a **constant-parameter filter**: this is pointed out by the weighting function, which is the same for any readout time t_m



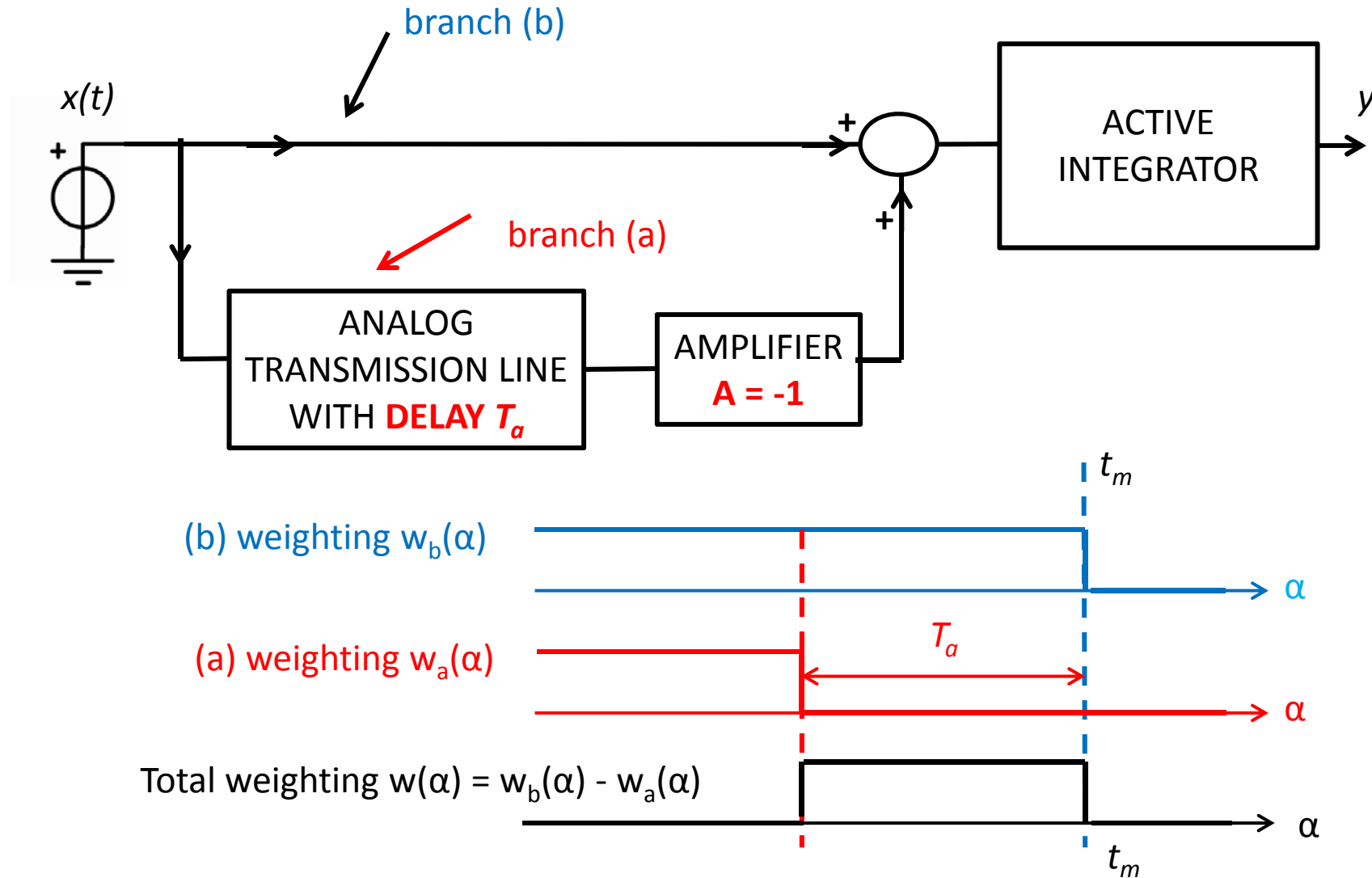The Mobile-Mean Filter is a constant-parameter filter



Mobile-mean filter versus RC-integrator

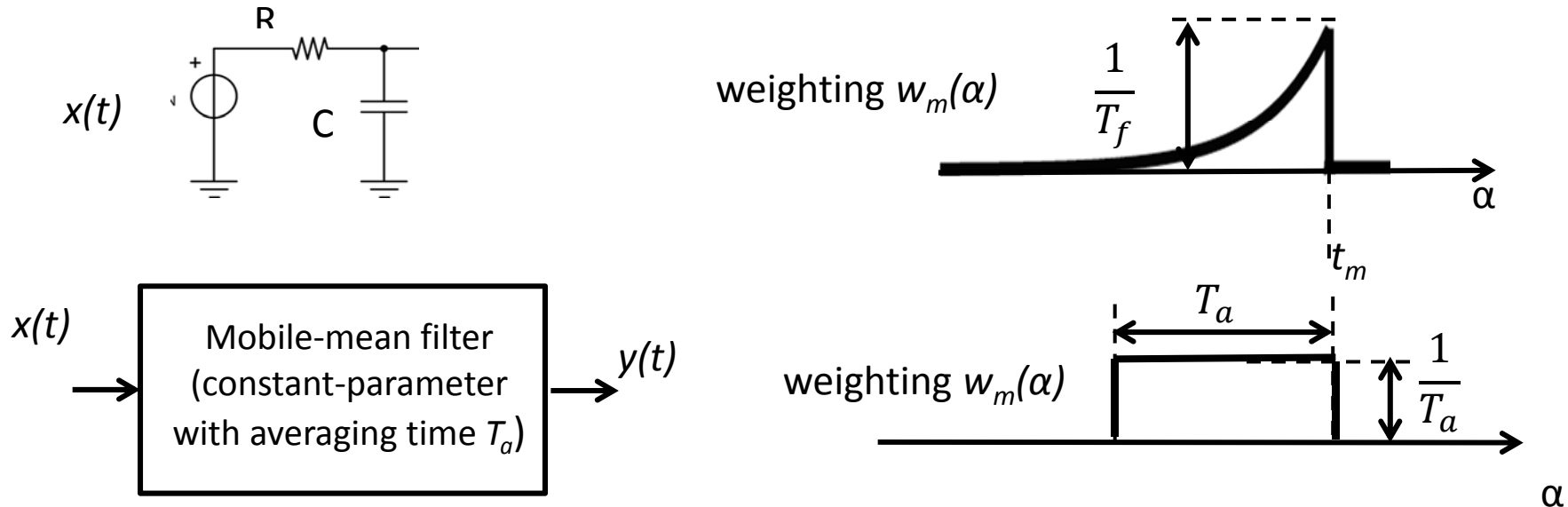

The mobile-mean filter produces an output $y(t_m)$ that is exactly the **mean value of the input x over the time interval T_a** preceding t_m .


When T_a is changed, the area of $w_m(\alpha)$ is kept constant, similarly to the case of the RC integrator when T_f is varied (the weight is reduced; the dc gain is kept constant)

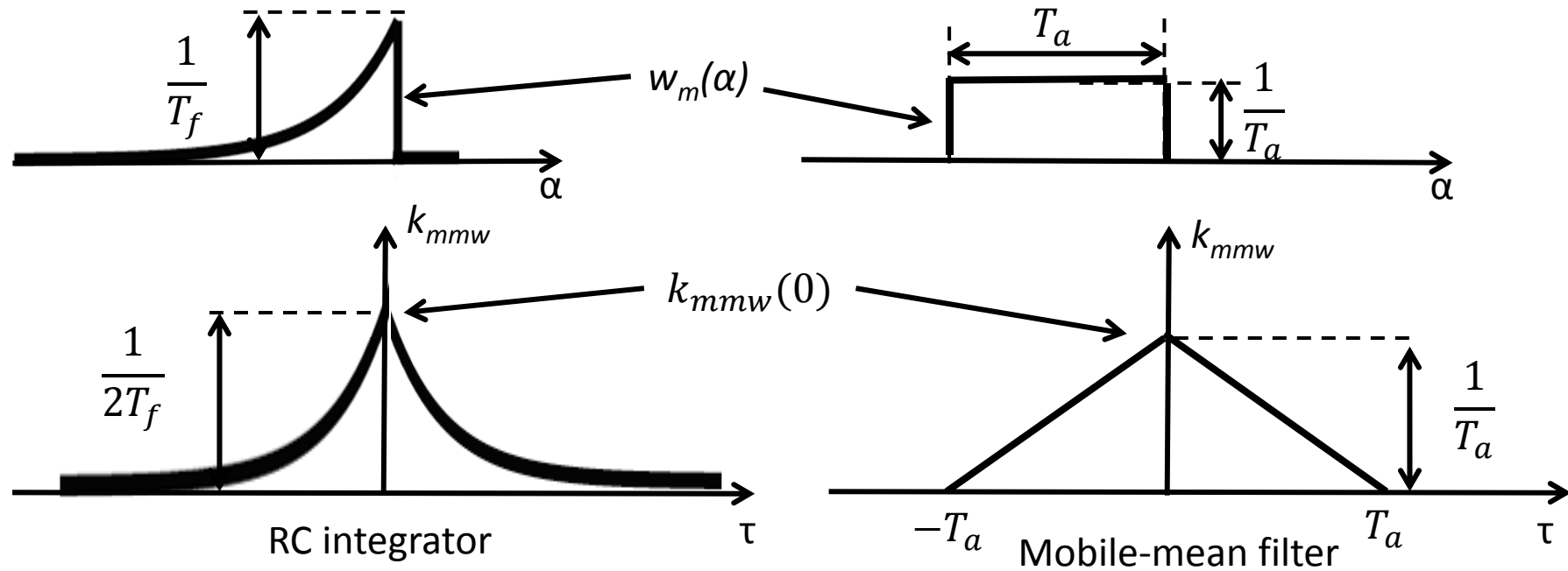Question: can we use a mobile-mean filter as equivalent to a given RC integrator for evaluating the result obtained by processing a signal with low-frequency content in presence of wide-band noise?

Answer: yes, the time T_a of the mobile-mean filter can be adjusted to produce equal output rms noise of the given RC integrator.



Mobile-mean filter equivalent to RC-integrator



Signal: the filters have **equal DC gain** (unity) and produce equal output with DC signal in.

Noise: for wide-band input noise the output noise is computed as

$$\overline{y^2} = S_{bB} \cdot k_{mmw}(0) = S_{bB} \cdot \int_{-\infty}^{\infty} w_m^2(\alpha) d\alpha$$


therefore, for having **equal output rms noise** it must be

$$T_a = 2T_f$$



Mobile-mean filter equivalent to RC-integrator

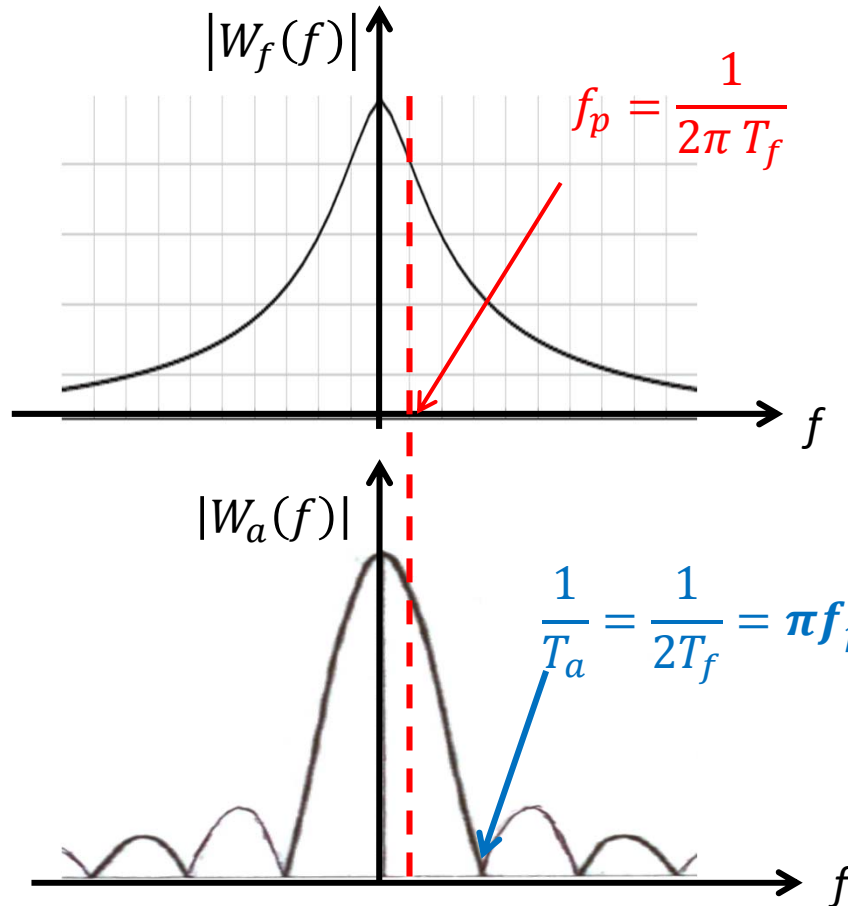The weighting functions of the two filters in frequency domain plotted with the same scales clearly illustrate the equivalence



RC integrator
with $RC = T_f$

$$|W_f(f)| = |H_f(f)| = \frac{1}{\sqrt{1 + (2\pi f T_f)^2}}$$

Mobile-mean filter
with averaging interval $T_a = 2T_f$
(and unity gain)

$$|W_a(f)| = |H_a(f)| = \frac{|\sin 2\pi f T_f|}{2\pi f T_f}$$



Band-Width and Correlation Time of Low-Pass filters




«Rectangular» approximations of real filters

- The noise bandwidth f_{fn} of a low-pass filter is currently employed for evaluating the output noise of low-pass filters in **frequency-domain** computations.
- A REAL filter that implements such a «rectangular weighting» in frequency DOES NOT EXIST: it would be a non-causal system, with δ -response that begins before the δ -pulse.
- The autocorrelation width T_{fn} is currently employed for evaluating the output noise of low-pass filters in **time-domain** computations.
- A REAL filter that implements such a «rectangular weighting» in time EXISTS: it is the mobile-mean filter with averaging time $T_a = T_{fn}$.
- There are, however, practical limitations to the implementation of mobile-mean filters, mainly due to the impractical features and limited performance of the real analog transmission lines with long delay, namely delay longer than a few tens of nanoseconds.



Other constant-parameter LPF

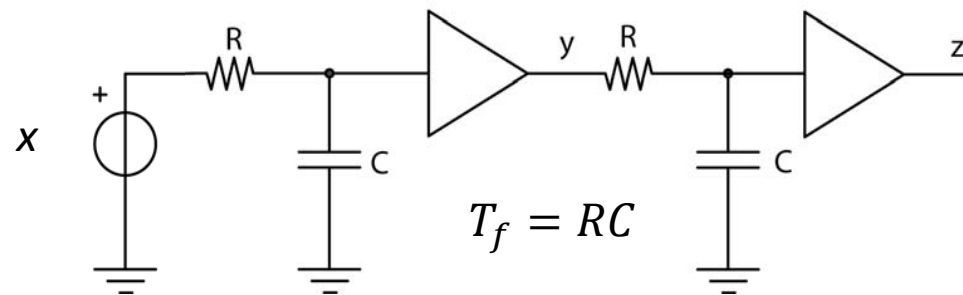For LPF filters with real poles, it is often easier to compute the noise bandwidth in time-domain rather than in frequency-domain, because it implies simple integrals (of exponentials and powers of t). Example: cascade of two identical RC cells



$$h(t) = \frac{t}{T_f^2} e^{-\frac{t}{T_f}}$$

$$\overline{z^2} = S_{bB} \cdot k_{hh}(0) = S_{bB} \cdot \int_{-\infty}^{\infty} h(t)^2 dt = S_{bB} \cdot \int_{-\infty}^{\infty} \left(\frac{t}{T_f^2}\right)^2 e^{-\frac{2t}{T_f}} dt$$

which integrated by parts gives

$$\overline{z^2} = S_{bB} \cdot \frac{1}{4T_f}$$

Since $\overline{z^2} = S_{bB} 2f_n$, the noise bandwidth f_n is

$$f_n = \frac{1}{8T_f}$$

