Sensors, Signals and Noise

COURSE OUTLINE

- Introduction
- Signals and Noise
- Filtering: High-Pass Filters 2 HPF2
- Sensors and associated electronics

1/f Noise and High-Pass Filters 2

- ➤ Measuring pulse signals in presence of 1/f noise with constant-parameter filters
- Basic constant-parameter High-Pass Filter (CR differentiator)
- Constant-Parameter High-Pass Filters in measurements of pulses in sequence
- > Switched-Parameter High-Pass Filter: the Baseline Restorer
- > Appendix: Band-limit of the high-pass CR differentiator for 1/f noise



Measuring pulse signals in presence of 1/f noise



Pulse signals in presence of 1/f noise

Case: amplitude measurement of **pulse** signals with **1/f** and wideband noise.

The classic approach to optimum filtering (to find first a noise-whitening filter and then a matched filter) is arduous in this case because 1/f noise

- sets a remarkably difficult mathematical problem
- makes the whitening filter difficult to design, not implementable with lumped circuit components, but with distributed parameters (distributed RC delay lines, etc.)

However, by noting that

- a) for 1/f noise the filtered power
- mainly depends on the span of the band-pass measured by the bandlimit ratio, hence it is markedly sensitive to the lower bandlimit level
- weakly depends on the shape of the filter weighting function
- b) for wideband noise the S/N
- depends on the span of the band-pass measured by the bandlimit difference, hence it is weakly sensitive to the lower bandlimit level
- markedly depends on the shape of the weighting function
 an alternative approach leading to quasi-optimum filtering can be devised



Pulses and 1/f noise: filtering in two-steps

FIRST STEP:

- Design a **main filter** for signal and wideband noise only (that is, considering non-existent the 1/f noise) and then
- Take then into account the 1/f component and evaluate the **additional noise power** that 1/f noise brings to the main filter output.

In the (lucky) cases where this 1/f noise power is smaller than the wide-band noise (or at least comparable), the main filter may be considered sufficient without further filtering.

Otherwise, if the addition due to 1/f noise is excessive, proceed to the

SECOND STEP:

• design an **additional filter** for limiting the 1/f noise power without worsening excessively the filtering of the wideband noise.

It is obviously a high-pass filter, which must combine the goal of

a) reducing efficiently the 1/f noise power

with the further requirements of

- b) limiting to tolerable level the increase of the filtered wide-band noise
- c) limiting to tolerable level the reduction of the output signal amplitude



Filtering Pulses and 1/f Noise: First Step

The issue is better clarified by considering as FIRST STEP the **optimum filter for signal and wide-band noise (or its approximation)** composed by

- Noise-whitening filter, with output white noise S_B and pulse signal. Let f_S be the upper band-limit and A the center-band amplitude of the pulse transform.
- Matched filter, which has weighting function matched to the pulse signal from the whitening filter and is therefore a low-pass filter with upper bandlimit f_s . The output has a signal with amplitude roughly $V_s \approx A f_s$ and band-limited white noise with band-limit f_s and power ___

$$\overline{n_B^2} \approx S_B f_S$$

For focusing the ideas, let's consider a well known specific case: filtering of pulse-signals from a high impedance sensor with an approximately optimum filter, i.e. with matched filter approximated by a constant-parameter RC integrator.

In this case, the output noise corresponding to the input wide-band noise is a white noise spectrum with band-limit set by a pole with time constant $RC=T_{nc}$



Filtering Pulses and 1/f Noise: Second Step

Let's now take into account also a 1/f noise source, which brings at the whitening filter output a significant 1/f spectral density $S_B f_C/f$.

At high frequency, the 1/f component is limited by the upper bandlimit f_s of the matched filter.

At low frequency, the 1/f component can be limited by a lower band-limit f_i set by an additional constant-parameter filter. With $f_i << f_S$ the output power of the 1/f noise can be evaluated as

$$\overline{n_{fn}^2} \approx S_B f_C \ln \left(\frac{f_S}{f_i}\right)$$

However, the constant-parameter high-pass filter operates also on the signal: it attenuates the low frequency components and thus causes a loss in pulse amplitude, hence a loss in S/N. The reduced amplitude is roughly evaluated as

$$V_S \approx A(f_S - f_i) = A f_S \left(1 - f_i / f_S\right)$$

For limiting the signal loss, f_i/f_s must be limited; e.g. for keeping loss < 5% it must be

$$f_i/f_S \le 0.05$$
 that is $\ln(f_S/f_i) \ge 3$



Filtering Pulses and 1/f Noise: Second Step

For reducing the 1/f noise to the white noise level or lower

$$S_B f_C \ln(f_S/f_i) \le S_B f_S$$

We need that

$$f_C \le \frac{f_S}{\ln(f_S/f_i)}$$

and since for keeping the signal loss <5% it must be $\ln(f_s/f_i) \ge 3$

we need to have

$$f_C < f_S/3$$

This means that the goal can be achieved only if the 1/f noise component is low or moderate. Note that f_c and f_s are data of the problem, they cannot be changed. In cases where f_c exceeds the above limit, a constant-parameter high-pass filter is NOT a suitable solution for reducing the 1/f noise power.


CONCLUSION: constant-parameter high-pass filters can be useful as additional filter for limiting the 1/f noise, but just in cases with moderate 1/f noise intensity, because of their detrimental effect on the signal pulse amplitude.



Basic constant-parameter High-Pass Filter (CR differentiator)



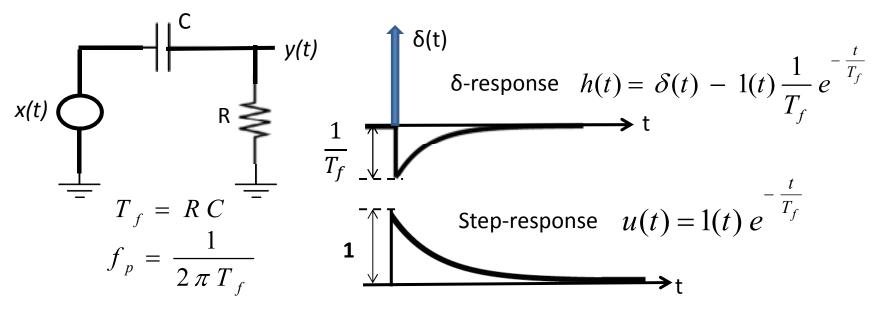
Basic High-Pass Filter (CR differentiator)



Transfer function

$$H(f) = \frac{j \, 2\pi f T_f}{1 + j \, 2\pi f T_f}$$

$$\left| H(f) \right|^2 = \frac{\left(2\pi f T_f \right)^2}{1 + \left(2\pi f T_f \right)^2}$$

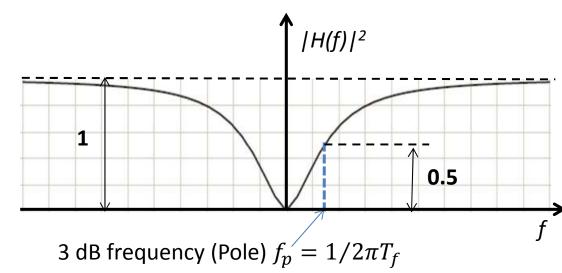



A view of High-Pass Filtering

The intuitive view

«High-Pass Filter = All-Pass - Low-Pass Filter»


is confirmed by Transfer function h(t) $h(t) = \delta(t) - 1(t) \frac{1}{T_f} e^{-\frac{t}{T_f}}$ δ -response Weighting function $w(\alpha) = \delta(\alpha) - 1(\alpha) \frac{1}{T_f} e^{-\frac{1}{2} (\alpha)}$ $w(\alpha)$ α



A view of High-Pass Filtering

The circuit mesh structure itself confirms that

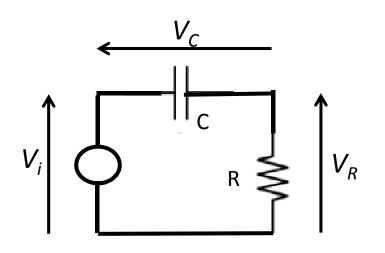«High-Pass Filter = All-Pass - Low-Pass Filter»



$$V_i$$
 = input voltage

$$V_C$$
 = low-pass filtered V

$$V_C = \text{low-pass filtered } V_i$$
 $V_R = \text{high-pass filtered } V_i$

Kirchoff's mesh voltage law

$$V_i = V_C + V_R$$

Therefore that is

$$V_R = V_i - V_C$$

High-pass filtered V_i = resistor voltage =

- = input voltage V_i capacitor voltage =
- = input voltage V_i Low-pass filtered V_i



Band-limit of CR differentiator

High-pass band-limit for White noise

Premise: with only a high-pass CR filter the white noise power $\overline{n_B^2}$ is divergent, therefore we consider here also a low-pass filter with band-limit $f_s >> 1/RC$.

The high-pass band-limit f_i of the CR filter with weighting function W(f) is defined by

$$\overline{n_B^2} = S_B \int_0^{f_S} |W(f)|^2 df = S_B \int_0^{f_S} \frac{(f/f_p)^2}{1 + (f/f_p)^2} df = S_B (f_S - f_i)$$

The computation of the integral can be avoided by recalling that CR high pass filter = all-pass – RC low-pass filter

and therefore

high-pass band-limit f_i of the CR filter = low-pass band-limit f_h of the RC filter

$$f_{iCR} = f_{hRC} = \frac{1}{4RC}$$



Band-limit of CR differentiator

High-pass band-limit for 1/f noise

Premise: with only a high-pass CR filter the 1/f noise power $\overline{n_f^2}$ is divergent, therefore we consider here also a low-pass filter with a high band-limit $f_s >> 1/RC$.

The high-pass band-limit f_{if} of the CR filter is defined by

$$\overline{n_f^2} = S_B f_c \int_0^{f_S} \frac{(f/f_p)^2}{1 + (f/f_p)^2} \frac{df}{f} = S_B f_c \int_{f_{if}}^{f_S} \frac{df}{f} = S_B f_c \ln(\frac{f_S}{f_{if}})$$

In this case the first integral is fairly easily computed* and shows that

$$f_{if} = \frac{f_p}{\sqrt{1 + \left(f_p / f_s\right)^2}}$$

that is, for $f_s >> f_p$

$$f_{if} \approx f_p = \frac{1}{2\pi RC}$$

^{*} See the appendix. Since the high-pass limit of the CR differentiator is also the low-pass limit of the RC integrator, we can avoid the computation for the latter (which is fairly difficult).

About band-limits and noise power

- The upper frequency limit f_s :
 - is necessary for limiting the white noise power
 - is useful also for limiting the 1/f noise power
 - the level of $f_{\mathcal{S}}$ is dictated by the pulse signal to be measured
- The lower frequency limit f_i :
 - is necessary for limiting the 1/f noise power,
 - the selected level of f_i is conditioned by the pulse signal, it cannot be arbitrary
 - however, the reduction of 1/f noise is significant even with fairly low f_i , that is, with f_S/f_i values that are high, but anyway finite.




Constant-Parameter High-Pass Filters in measurements of pulses in sequence



CR filter and pulse sequence

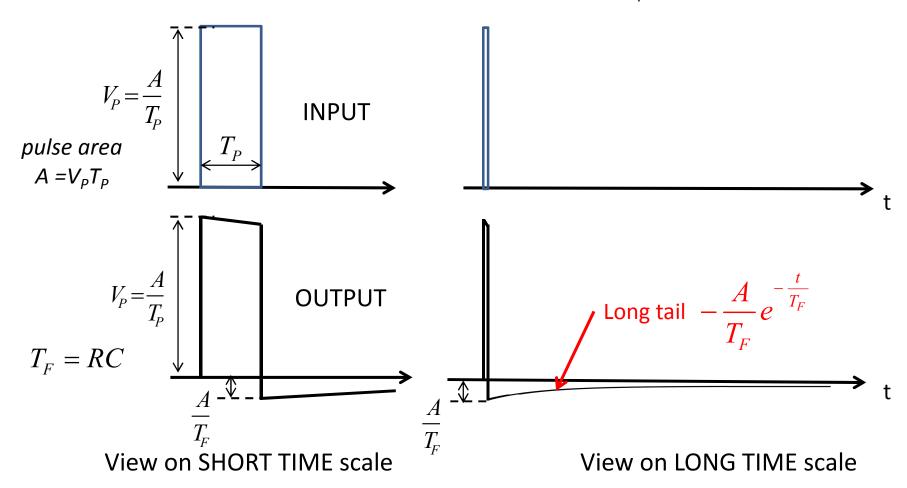
Let's look in detail the effect of a high-pass filter (RC = T_F) on a pulse signal



NB: DC transfer of CR is zero → net area of the output signal is zero





CR filter and pulse sequence

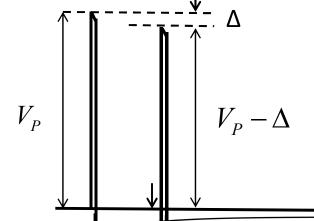

A pulse that follows a previous one within a fairly short time interval ($T_D < 5 T_F$) steps on the slow tail of the first pulse. Therefore, it starts from a down-shifted baseline, so that the amplitude measured for it is smaller than the true one.

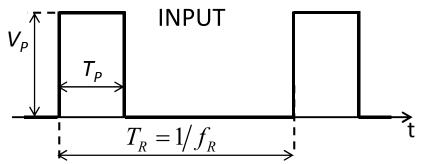For periodic pulses with fairly short repetition period $T_R << T_F$, the superposition of slow pulse-tails shifts down the baseline by a V_S that makes zero the net area of the output signal



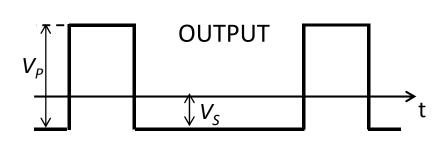

Repetition-rate-dependent baseline-shift $V_S = V_P \frac{T_P}{T_R} = A f_R$



Drawbacks of the CR differentiator filter

The high-pass filtering (differentiator action) of the CR filter has **MIXED effects.**

- The effect **on noise is ADVANTAGEOUS:** by cutting off the low frequencies it markedly decreases the 1/f noise power (and mildly reduces the white noise power)
- The effect on the signal is DISADVANTAGEOUS:
- \succ it decreases the signal amplitude by cutting off the low frequencies of the signal , hence f_i must be kept low ($f_i << f_s$ of the pulse) in order to limit the signal loss. However, this limits also the reduction of 1/f noise
- it generates slow tails after the pulses, which shift down the baseline and thus cause an error in the measured amplitude of a following pulse
- ➤ With a **periodic** sequence of equal pulses, all pulses find the same baseline shift. The amplitude error is constant, sistematically dependent on the repetition rate.
- ➤ With **random-repetition** pulses (e.g. pulses from ionizing radiation detectors) the pulses occur randomly in time. Hence the random superposition of tails produces a randomly fluctuating baseline shift. The resulting amplitude error is random: in this case the effect is equivalent to that of an additional noise source.

CONCLUSION: a differentiator action is **desirable on noise**, but **NOT on the signal**.


WANTED: not a constant-parameter differentiator, but a true Base-Line Restorer (BLR)

Switched-Parameter High-Pass Filter: the Baseline Restorer



Baseline Restorer (BLR) principle: switched CR

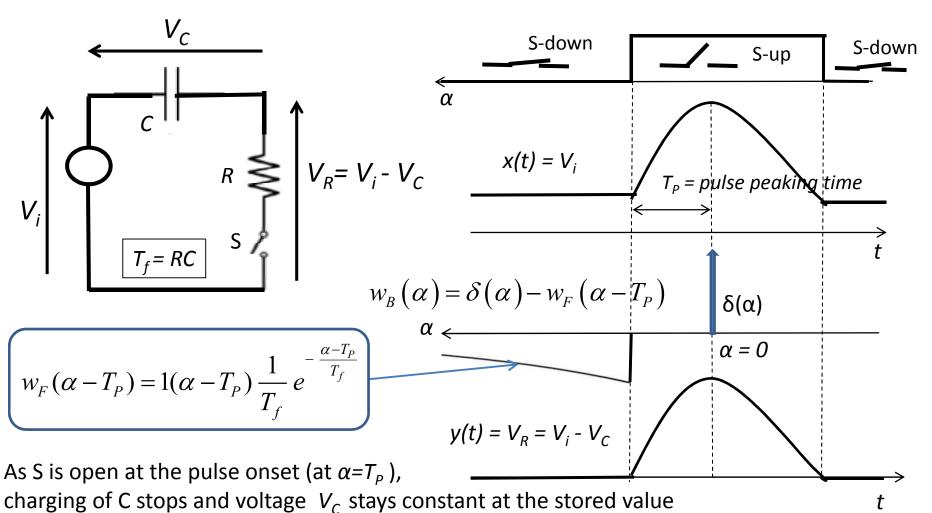
High-pass filtering action on the noise and NOT on the signal: switched-parameter CR filter with CR $\rightarrow \infty$ when signal is present, finite CR = T_F when no pulse is present




Comparing constant CR filter and BLR

SWITCHED-PARAMETER FILTER

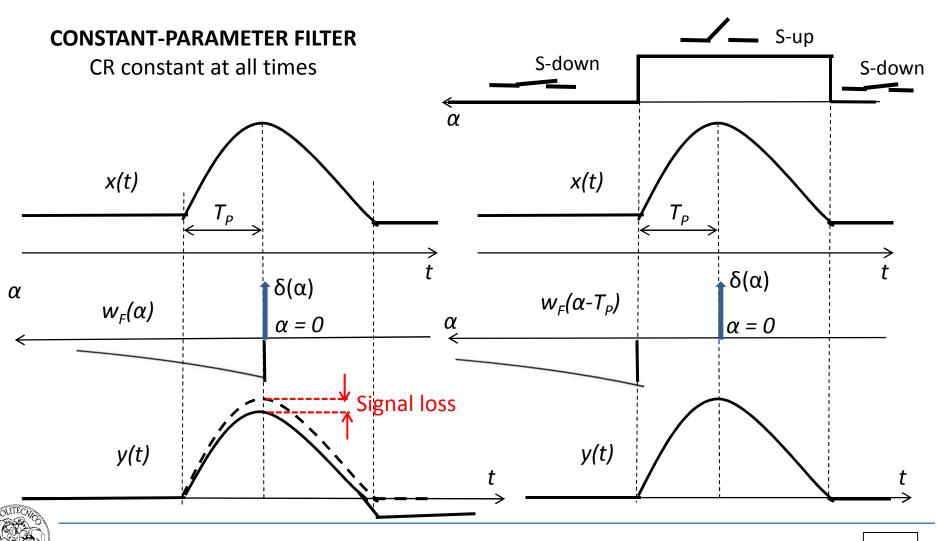with S-up R $\rightarrow \infty$ and CR $\rightarrow \infty$



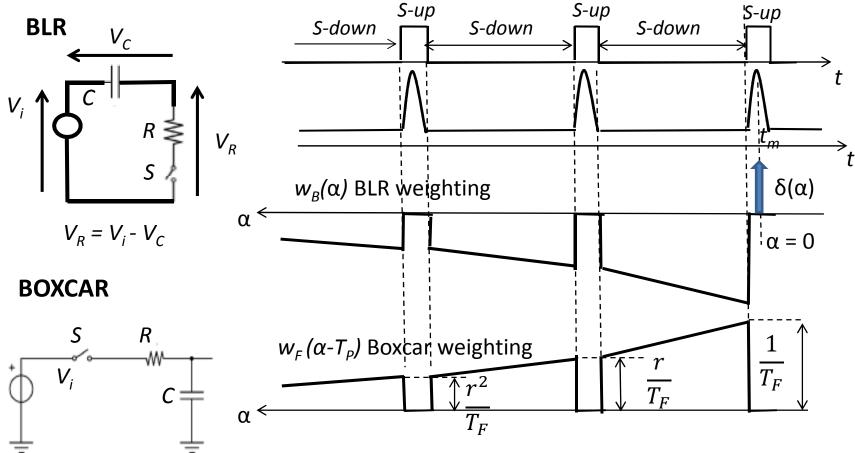BLR = All Pass - Low-Pass Boxcar Integrator




BLR weighting = All Pass – Low-pass Boxcar weighting

$$W_B(\alpha) = \delta(\alpha) - W_F(\alpha - T_P)$$



BLR weighting in frequency

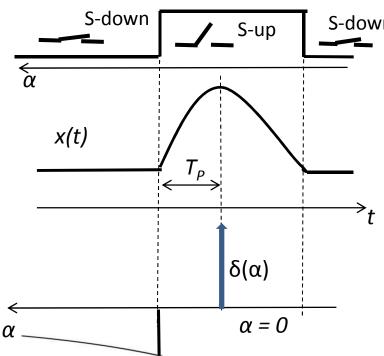

BLR principle is alike filtered zero-setting, but with a basic advantage: much shorter T_p much higher band-limit f_{if} (high-pass)

(the BLR switch is electronically controlled, the interval T_P can be very short)

BLR weighting = All Pass – Low-pass

$$w_{B}(\alpha) = \delta(\alpha) - w_{F}(\alpha - T_{P})$$

Low-pass weighting in frequency:

$$W_F(\omega) = F[w_F(\alpha)] = R_F(\omega) + i I_F(\omega)$$

BLR weighting in frequency:

$$W_B(\omega) = 1 - e^{j\omega T_P} W_F(\omega) = 1 - [\cos \omega T_P - j\sin \omega T_P] \cdot [R_F + jI_F] =$$

$$= [1 - R_F \cos \omega T_P - I_F \sin \omega T_P] - j[I_F \cos \omega T_P - R_F \sin \omega T_P]$$



BLR weighting in frequency

BLR weighting for noise:

$$\begin{aligned} & \left| W_B(\omega) \right|^2 = [1 - R_F \cos \omega T_P - I_F \sin \omega T_P]^2 + [I_F \cos \omega T_P - R_F \sin \omega T_P]^2 = \\ & = 1 + R_F^2 + I_F^2 - 2R_F \cos \omega T_P + 2I_F \sin \omega T_P = \\ & = 1 + \left| W_F \right|^2 - 2R_F \cos \omega T_P - 2I_F \sin \omega T_P \end{aligned}$$

Let's consider just cases where the interval between pulses is much longer than T_F so that $1 - \frac{\alpha}{2}$

$$W_F(\alpha) = 1(\alpha) \frac{1}{T_f} e^{-\frac{\alpha}{T_f}}$$
 and $W_F(\omega) = \frac{1}{1 + j\omega T_F}$

and therefore

$$|W_B(\omega)|^2 = 1 + \frac{1}{1 + \omega^2 T_F^2} - 2\frac{1}{1 + \omega^2 T_F^2} \cos \omega T_P + 2\omega T_F \cdot \frac{1}{1 + \omega^2 T_F^2} \sin \omega T_P$$



BLR cutoff

In the low-frequency region $\omega \ll \frac{1}{T_P}$ with the approximations $\sin \omega T_P \approx \omega T_P$ $\cos \omega T_P = 1 - \frac{\omega^2 T_P^2}{2}$

$$\sin \omega T_P \approx \omega T_P$$

$$\cos \omega T_P = 1 - \frac{\omega^2 T_P^2}{2}$$

we get

$$|W_B(\omega)|^2 \approx 1 + \frac{1}{1 + \omega^2 T_F^2} - \frac{2}{1 + \omega^2 T_F^2} + \frac{\omega^2 T_P^2}{1 + \omega^2 T_F^2} + 2\frac{\omega^2 T_P T_F}{1 + \omega^2 T_F^2} =$$

$$= \frac{\omega^2 (T_P + T_F)^2}{1 + \omega^2 T_F^2} = \frac{\omega^2 T_F^2}{1 + \omega^2 T_F^2} \left(1 + \frac{T_P}{T_F}\right)^2$$


and in the lower region $\omega \ll \frac{1}{T_{\scriptscriptstyle E}} \ll \frac{1}{T_{\scriptscriptstyle P}}$

$$\left|W_B(\omega)\right|^2 \approx \omega^2 \left(T_P + T_F\right)^2$$

That is, the BLR has a cutoff equivalent to a CR high-pass with RC= $T_P + T_F$



BLR vs. CR High-Pass Filter: Cut-Off

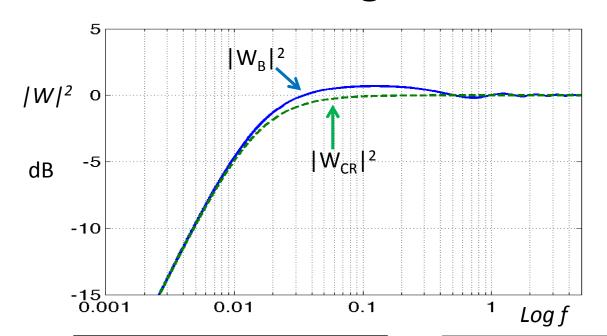

BODE DIAGRAM highlights the low-freq cutoff

Example: BLR with $T_P = 1$ and $T_F = 10$ CR filter with RC = $T_P + T_F$

$$f \ll 1/T_F$$
 (i.e. $f \ll 0.1$ in the example)

$$\left|W_{B}(\omega)\right|^{2} \approx \omega^{2} \left(T_{P} + T_{F}\right)^{2}$$
$$\left|W_{CR}(\omega)\right|^{2} \approx \omega^{2} R^{2} C^{2}$$


$$\left|W_{CR}(\omega)\right|^2 \approx \omega^2 R^2 C^2$$

$$1/T_F < f << 1/T_P$$
(i.e. $f << 1$ in the example)
$$\left|W_B(\omega)\right|^2 \approx \frac{\omega^2 \left(T_P + T_F\right)^2}{1 + \omega^2 T_F^2}$$

$$\left|W_{CR}(\omega)\right|^2 = \frac{\omega^2 R^2 C^2}{1 + \omega^2 R^2 C^2}$$



BLR vs. CR High-Pass Filter: White Noise

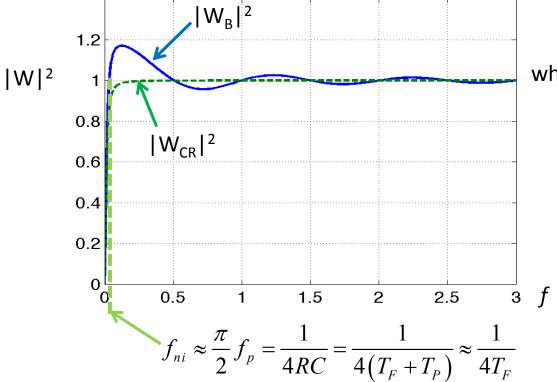

LIN –LIN DIAGRAM
highlights
white noise power \propto area of $|W|^2$


Example: BLR with $T_P = 1$ and $T_F = 10$ CR filter with $RC = T_P + T_F$

 f_{ni} = BLR high-pass band-limit for white noise. Note that:

- f_{ni} is equal to that of the equivalent CR High-pass filter
- f_{ni} is equal to bandlimit of the low-pass section in the BLR circuit



BLR vs. CR High-Pass Filter: 1/f Noise

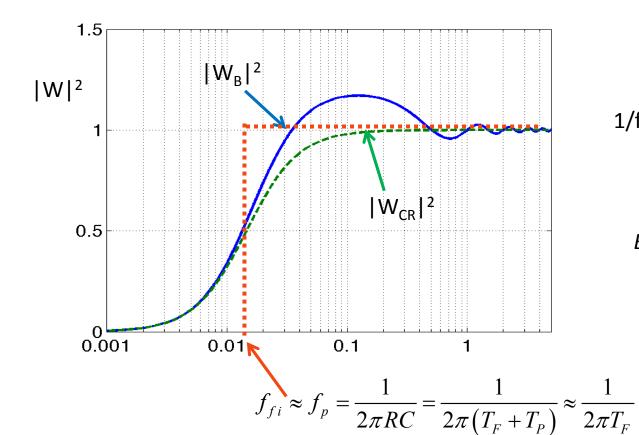

LIN –LOG DIAGRAM
highlights

1/f noise power ∝ area of |W|²

Example: BLR with $T_p = 1$ and $T_F = 10$ CR filter with $RC = T_p + T_F$

 f_{fi} = BLR high-pass band-limit for 1/f noise. Note that:

- f_{fi} is equal to that of the equivalent CR High-pass filter
- f_{fi} is equal to bandlimit of the low-pass section in the BLR circuit



Selection of the BLR parameters

The BLR filtering is ruled by:

- 1. T_P time delay from switch opening to pulse-amplitude measurement. There is **no choice**: T_P is equal to the rise time from pulse onset to peak. In fact, T_P can't be shorter than the rise of the pulse signal and should be as short as possible for filtering effectively of the 1/f noise.
- 2. $T_F = RC$ differentiation time constant: to be selected for optimizing the overall filtering of noise. The question is: how should T_F be selected for
- a) providing a good reduction of the 1/f noise power and
- b) avoiding to enhance significantly the white noise power


Since the BLR cutoff is set by $1/(T_P + T_F)$, a very short T_F might look advisable, but it is not: a BLR with $T_F << T_P$ operates like a CDS, hence it doubles the white noise and remarkably enhances also the 1/f noise above the cutoff frequency.

In the following discussion about the T_F selection, for focusing the ideas we will refer to a specific case: signals from a high impedance sensor processed by an approximately optimum filter, namely a CR-RC filter. The output corresponding to the input wide-band noise is a white spectrum band-limited by a simple pole. Such a situation is met in practice also in many other cases.

A better insight in the issue is gained with a time-domain analysis of BLR filtering




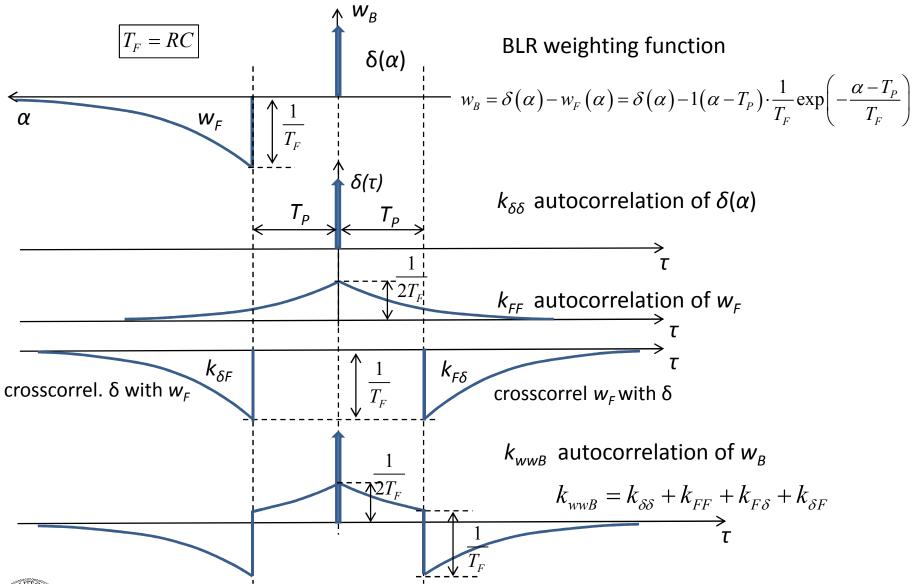BLR Filtering of Noise: time-domain analysis





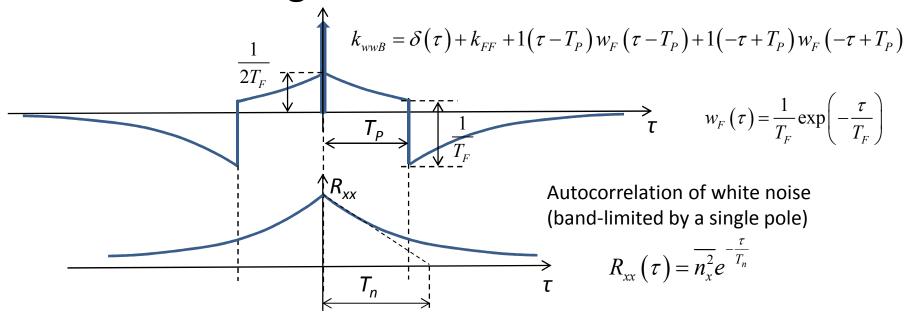BLR Filtering of Band-Limited White Noise



$$\overline{n_B^2} = \int_{-\infty}^{\infty} R_{xx}(\tau) k_{wwB}(\tau) d\tau = R_{xx}(0) + 2 \int_0^{\infty} R_{xx}(\tau) \frac{1}{2} w_F(\tau) d\tau - 2 \int_T^{\infty} R_{xx}(\tau) w_F(\tau - T_P) d\tau =$$

$$= R_{xx}(0) + \int_{-\infty}^{\infty} R_{xx}(\tau) \frac{1}{2} w_F(\tau) d\tau - 2 \int_0^{\infty} R_{xx}(\beta + T_P) w_F(\beta) d\beta$$

Denoting

$$r_{xx}(\tau) = \frac{R_{xx}(\tau)}{R_{xx}(0)} = \frac{R_{xx}(\tau)}{\overline{n_x^2}}$$

We have

$$\overline{n_B^2} = \overline{n_x^2} \left\{ 1 + \int_{-\infty}^{\infty} r_{xx} \left(\tau \right) \frac{1}{T_F} e^{-\frac{\tau}{T_F}} d\tau - 2 \int_{0}^{\infty} r_{xx} \left(\beta + T_P \right) \frac{1}{T_F} e^{-\frac{\beta}{T_F}} d\beta \right\}$$



BLR Filtering of Band-Limited White Noise

$$\overline{n_{B}^{2}} = \overline{n_{x}^{2}} \left\{ 1 + \int_{-\infty}^{\infty} r_{xx}(\tau) \cdot \frac{1}{T_{F}} e^{-\frac{\tau}{T_{F}}} d\tau - 2 \int_{0}^{\infty} r_{xx}(\beta + T_{P}) \cdot \frac{1}{T_{F}} e^{-\frac{\beta}{T_{F}}} d\beta \right\} =$$

$$= \overline{n_{x}^{2}} \left\{ 1 + \frac{1}{T_{F}} \int_{-\infty}^{\infty} e^{-\tau \left(\frac{1}{T_{F}} + \frac{1}{T_{n}}\right)} d\tau - 2 e^{-\frac{T_{P}}{T_{n}}} \frac{1}{T_{F}} \int_{0}^{\infty} e^{-\beta \left(\frac{1}{T_{F}} + \frac{1}{T_{n}}\right)} d\beta \right\} =$$

$$= \overline{n_{x}^{2}} \left\{ 1 + \frac{T_{n}}{T_{n} + T_{F}} - 2 e^{-\frac{T_{P}}{T_{n}}} \frac{T_{n}}{T_{n} + T_{F}} \right\}$$

and finally


$$\left| \overline{n_B^2} = \overline{n_x^2} \left[1 + \frac{T_n}{T_n + T_F} \left(1 - 2e^{-\frac{T_P}{T_n}} \right) \right] \right|$$

With **fast differentiation**, i.e. with $T_F \ll T_n$, it is quantitatively confirmed that the BLR acts like a CDS with $T=T_P$

$$\overline{n_B^2} \approx 2\overline{n_x^2} \cdot \left(1 - e^{-\frac{T_P}{T_n}}\right)$$



BLR Filtering with fast differentiation

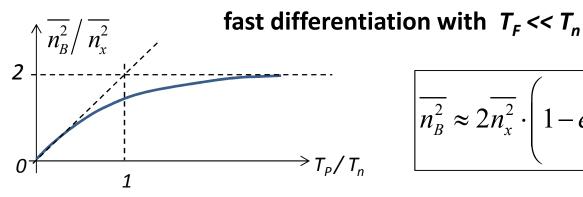

$$\overline{n_B^2} \approx 2\overline{n_x^2} \cdot \left(1 - e^{-\frac{T_P}{T_n}}\right)$$

With $T_F \ll T_n$ the effect of BLR on **band-limited white noise** depends on how long is the correlation time T_n with respect to the delay T_P

with **short correlation time** (wide band) the noise is **doubled**:

with
$$T_n < T_P/5$$
 it is $\overline{n_B^2} \approx 2\overline{n_x^2}$

with **moderate correlation time** (moderately wide band) the noise is enhanced:


with
$$T_n \approx T_P/2$$
 it is $\overline{n_B^2} \approx 1,73 \, \overline{n_x^2}$

only with long correlation time (low-frequency band) the noise is attenuated*:

with
$$T_n > 10T_P$$
 it is $\overline{n_B^2} \approx \overline{n_x^2} \cdot 2\frac{T_P}{T_n} < 0, 2\overline{n_x^2}$


* note that anyway the level is **double** of that given by a simple CR filter with equal cutoff, that is with $T_F = RC = T_P$

BLR Filtering with fast differentiation

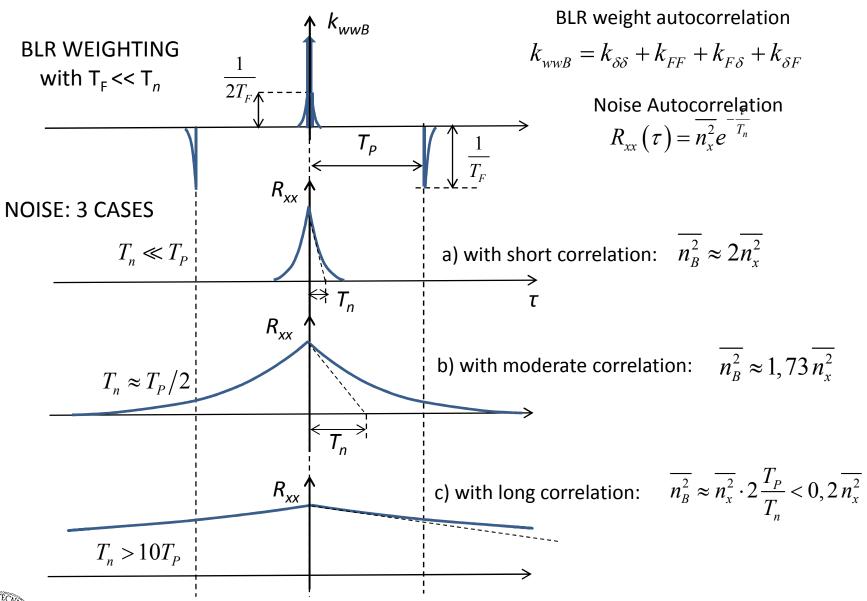



BLR Filtering with slow differentiation

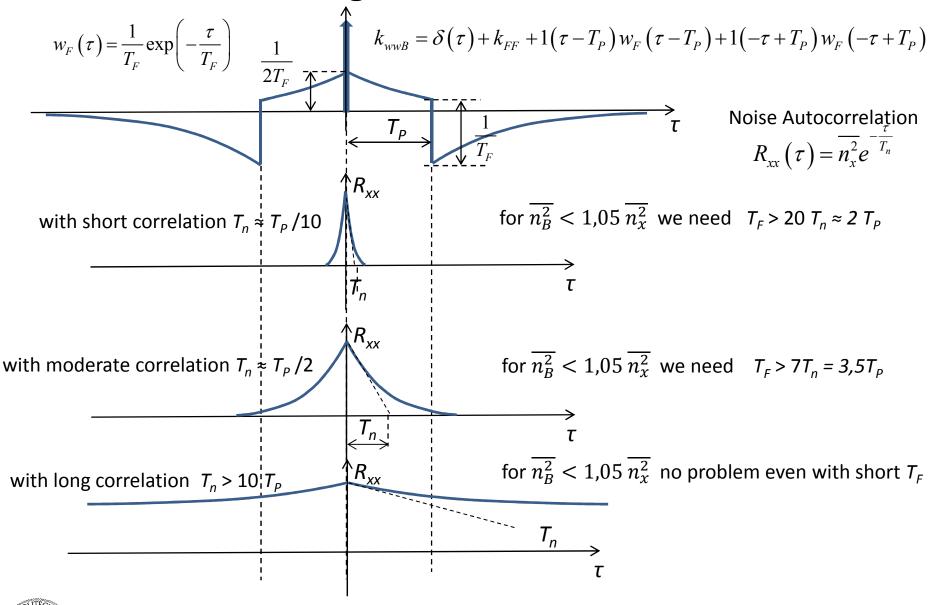



BLR Filtering with slow differentiation

With T_F NOT negligible with respect to T_n , the effect on white noise depends also on the size of T_F compared to T_n and T_P . A long T_F can limit the white noise enhancement

$$\overline{n_B^2} = \overline{n_x^2} \left[1 + \frac{T_n}{T_n + T_F} \left(1 - 2e^{-\frac{T_P}{T_n}} \right) \right]$$

Let's evaluate how long must be T_F in the various cases of noise correlation

• with short correlation time $T_n \approx T_P / 10$ it is

$$\overline{n_B^2} \approx \overline{n_x^2} \left(1 + \frac{T_n}{T_n + T_F} \right)$$

for keeping $\overline{n_B^2} < 1.05 \, \overline{n_x^2}$ we need $T_F > 20 \, T_n \approx 2 \, T_P$

• with moderate correlation time $T_n \approx T_P/2$ it is

$$\overline{n_B^2} \approx \overline{n_x^2} \left[1 + \frac{T_n}{T_n + T_F} \left(1 - \frac{2}{e^2} \right) \right] = \overline{n_x^2} \left[1 + 0,73 \frac{T_n}{T_n + T_F} \right]$$

for keeping $\overline{n_B^2} < 1.05 \, \overline{n_x^2}$ in this case we need $T_F > 7T_n = 3.5T_P$



BLR Filtering with slow differentiation

• with **long correlation time** $T_n > 10 T_P$ it is

$$\overline{n_B^2} \approx \overline{n_x^2} \left[1 - \frac{T_n}{T_n + T_F} \right] = \overline{n_x^2} \frac{T_F}{T_n + T_F}$$

No problem with such a low-frequency noise: it is attenuted by the BLR just as by a CR constant-parameter filter (with equal time constant $T_F = RC$)

The most interesting case for us is noise with moderate T_n . In fact, when the BLR works on the output of an optimum (or approximate-optimum) filter for wideband noise, the correlation time T_n and delay T_p are comparable, since they are both closely related to the band-limit of the signal pulse.

• We conclude that for avoiding enhancement of the white noise it is necessary to select a fairly slow BLR differentiation, i.e. a fairly long T_F

$$T_F \ge 5 T_P$$

• This approach is satisfactory also for filtering the 1/f noise, notwithstanding that making T_F longer than T_P shifts down the BLR cutoff frequency, hence reduces the attenuation of 1/f noise. This is counterbalanced by the fact that the enhancement of 1/f noise at frequencies above the cutoff is limited by the low-pass filtering in the baseline subtraction, whereas with short T_F it is remarkable.



BLR in summary

- The BLR is a high-pass filter that acts on noise and disturbances without affecting the pulse signal
- The BLR is a switched-parameter filter: the low-pass section within the high-pass filter structure is a boxcar integrator that acquires the baseline only in the intervals free from pulses
- The BLR can thus establish a high-pass band-limit at a high value (suitable for reducing efficiently the 1/f noise output power) without causing the signal loss suffered with a constant-parameter high-pass filter having the same band-limit
- The high-pass band-limit enforced by the BLR is given (with good approximation)
 by the low-pass bandlimit of the low-pass section in the BLR circuit structure
- The combination of: (1) optimum filter designed for the case of pulse signal in presence of wideband noise only (i.e. without 1/f noise) and (2) BLR specifically designed (for reducing the actual 1/f noise without worsening the wide-band noise) provides in most cases a quasi-optimum filtering solution.



Appendix: Band-limit of the high-pass CR differentiator for 1/f noise

Premise: with only a high-pass CR filter the 1/f noise power n_f^2 is divergent, therefore we consider here also a low-pass filter with very high band-limit $f_s >> f_p = 1/2\pi RC$.

$$\overline{n_f^2} = S_B f_c \int_0^{f_S} \frac{\left(f/f_p\right)^2}{1 + \left(f/f_p\right)^2} \frac{df}{f} \quad \text{equivalent to} \quad \overline{n_f^2} = S_B f_c \int_{f_{if}}^{f_S} \frac{df}{f} = S_B f_c \ln(\frac{f_S}{f_{if}})$$

By changing variable
$$\frac{f}{f_p} = x$$
 $\frac{df}{f} = \frac{dx}{x}$ $\frac{f_S}{f_p} = x_S$

We have
$$\overline{n_f^2} = S_B f_c \int_0^{x_S} \frac{x^2}{1+x^2} \frac{dx}{x} = \frac{S_B f_c}{2} \int_0^{x_S} \frac{2x}{1+x^2} dx = \frac{S_B f_c}{2} \int_0^{x_S} \frac{1}{1+x^2} d(x^2)$$

and by setting
$$x^2 = y$$
 $2xdx = dy$ $x_S^2 = y_S$

We obtain
$$\overline{n_f^2} = \frac{S_B f_c}{2} \int_0^{y_S} \frac{1}{1+y} dy = \frac{S_B f_c}{2} \left| \ln(1+y) \right|_0^{y_S} = \frac{S_B f_c}{2} \ln(1+y_S)$$



Appendix: Band-limit of the high-pass CR differentiator for 1/f noise

$$\overline{n_f^2} = \frac{S_B f_c}{2} \ln(1 + y_S) = S_B f_c \ln \sqrt{1 + y_S} = S_B f_c \ln \sqrt{1 + \left(\frac{f_S}{f_p}\right)^2}$$

Since the high-pass band-limit f_{if} is defined by

$$\overline{n_f^2} = S_B f_c \int_{f_{if}}^{f_S} \frac{df}{f} = S_B f_c \ln(\frac{f_S}{f_{if}})$$

it is
$$\frac{f_S}{f_{if}} = \sqrt{1 + \left(\frac{f_S}{f_p}\right)^2}$$
 and therefore $f_{if} = \frac{f_p}{\sqrt{1 + \left(f_p/f_s\right)^2}}$

and taking into account that $f_s >> f_p$ we have finally

$$f_{if} \approx f_p = \frac{1}{2\pi RC}$$

